

# 1 LABORATION 1 - COMBINATORIAL CIRCUITS

In the laboration, we build the first component of the microprocessor, the ALU. We will describe the design using RTL-modelling in System Verilog. We also exercise how to build a basic testbench to check its functionality.

The lab only requires simulation in Questasim, Modelsim or other HDL simulation tool.

## 1.1 TASKS

To complete this lab you must successfully complete the following tasks:

1) Build an RTL model of the ALU. The definition of the module is given in the file `ALU.sv`. The ALU should use 2's complement arithmetic. The implementation has to follow the schematic shown in figure 1.1.

 


FIGURE 1.1. ALU SCHEMATIC.

2) The ALU should implement the following functions:

Operation		Outputs	Flags		
Name	Code	Y	O	N	Z
ADD	000	A+B	Is active (=1) if the result of an ADD- or SUB- operation gives the wrong sign bit on Y.	Is active (=1) if the result on Y is negative.	Is active (=1) if the all bits in Y are 0.
SUB	001	A-B			
AND	010	A AND B			
OR	011	A OR B			
XOR	100	A XOR B			
INC	101	A+1			
MOVA	110	A			
MOVB	111	B			

3) The ALU has two generic inputs A and B (n-bit), one OP code input (3 bits)

4) The ALU has 1 generic n-bit output and a 3-bit flag output ONZ (**\*\*make sure that you use the specific order, O is the MSB and Z is the LSB\*\***)

5) Build a testbench that verifies the functionality of the ALU.

1) The testbench has to check all possible functions of the ALU.

2) A skeleton for the ALU testbench is given in the file `ALU\_tb.sv`

3) Use randomized inputs to test your design.

4) Create an automatic check to make sure that all functions are working correctly.

## 1.2 DELIVERABLES:

1) All your files describing the ALU design

2) All your files that implement your testbench