

# Pass/Fail Homework 1

Use the last 3 digits of your personal number (PN) to select which question you have to answer. Modulo divide your 3 digits with the number of questions, in this case, 8, plus 1. The resulting number is the question that you should answer.

**!!! (PN mod 8) + 1 !!!**

For example, if your PN ends in 730, then  $(730 \bmod 8) + 1 = 3$ , meaning you must answer question 3.

Make sure you comment on the top of each file you submit, your PN, name and the question you are answering.

**!!! IMPORTANT !!!**

**If you answer the wrong question, your submission will be invalid.**

**We can call you to explain your solution. If you cannot explain your answer, the homework will be invalid!**

**KTH has a zero-tolerance policy against cheating.**

<https://www.kth.se/en/student/stod/studier/fusk-1.997287>


**If you have questions or need clarifications, you can ask in the discussion forum in Canvas.**

## QUESTIONS
 
### 1.1 QUESTION 1

Model using HDL a look-up table **using a 1-to-16 de-multiplexer** that can act as a 4-bit one-hot decoder. The design should take as input a 4-bit binary value and output the one-hot equivalent. The definition of the module is given below.

```
module decoder (  
    input  logic [3:0] binary,  
    output logic [15:0] one_hot  
);  
    // ...  
    // Add your description here  
    // ...  
endmodule
```



## 1.2 QUESTION 2


Model using HDL a design that can act as a 4-to-2-bit encoder. The design should take as input a 4-bit one-hot number and output the equivalent binary value. The table below shows the functionality of a simple 4-to-2-bit encoder. Note that the '-' in the table signifies don't-care values. The don't care values can be either 0 or 1. The definition of the module is given below.

| 4 to 2 Simple Encoder |                |                |                |                |                |       |
|-----------------------|----------------|----------------|----------------|----------------|----------------|-------|
| I <sub>3</sub>        | I <sub>2</sub> | I <sub>1</sub> | I <sub>0</sub> | O <sub>1</sub> | O <sub>0</sub> | Valid |
| -                     | -              | -              | -              | -              | -              | 0     |
| 0                     | 0              | 0              | 0              | -              | -              | 0     |
| 0                     | 0              | 0              | 1              | 0              | 0              | 1     |
| 0                     | 0              | 1              | 0              | 0              | 1              | 1     |
| 0                     | 1              | 0              | 0              | 1              | 0              | 1     |
| 1                     | 0              | 0              | 0              | 1              | 1              | 1     |

```

module one_hot_encoder (
    input logic [3:0] one_hot,
    output logic [1:0] binary,
    output valid
);
    // ...
    // Add your description here
    // ...
endmodule

```

 


## 1.3 QUESTION 3

Model using HDL a design that uses **16-to-1 multiplexers** and implements a 4-bit binary to BCD (Binary-coded decimal) encoder. The BCD encoding can be seen in the following table. The module definition is also seen below.

| Decimal | Binary | BCD |   |   |   | Carry |
|---------|--------|-----|---|---|---|-------|
|         |        | 8   | 4 | 2 | 1 |       |
| 0       | 0000   | 0   | 0 | 0 | 0 | 0     |
| 1       | 0001   | 0   | 0 | 0 | 1 | 0     |
| 2       | 0010   | 0   | 0 | 1 | 0 | 0     |
| 3       | 0011   | 0   | 0 | 1 | 1 | 0     |

|    |      |   |   |   |   |   |
|----|------|---|---|---|---|---|
| 4  | 0100 | 0 | 1 | 0 | 0 | 0 |
| 5  | 0101 | 0 | 1 | 0 | 1 | 0 |
| 6  | 0110 | 0 | 1 | 1 | 0 | 0 |
| 7  | 0111 | 0 | 1 | 1 | 1 | 0 |
| 8  | 1000 | 1 | 0 | 0 | 0 | 0 |
| 9  | 1001 | 1 | 0 | 0 | 1 | 0 |
| 10 | 1010 | 0 | 0 | 0 | 0 | 1 |
| 11 | 1011 | 0 | 0 | 0 | 1 | 1 |
| 12 | 1100 | 0 | 0 | 1 | 0 | 1 |
| 13 | 1101 | 0 | 0 | 1 | 1 | 1 |
| 14 | 1110 | 0 | 1 | 0 | 0 | 1 |
| 15 | 1111 | 0 | 1 | 0 | 1 | 1 |

 

```

module bin2bcd (
    input logic [3:0] binary,
    output logic [3:0] bcd,
    output logic carry
);
    // ...
    // Add your description here
    // ...
endmodule

```

## 1.4 QUESTION 4


Model a design using HDL that implements an 8-bit unsigned carry select adder (CSA). The CSA should be built using 4-bit adders. The design of the adder is given to you. The definition of the module can be seen below.

```

module CSA_8 (
    input logic [7:0] A, B,
    output logic [7:0] sum,
    output logic carry
);
    // ...
    // Add your description here
    // ...
endmodule

module adder_4 (
    input logic [3:0] A, B,
    output logic [3:0] sum,
    output logic carry
);
    // ...
    assign {carry, sum} = A+B;
endmodule


```

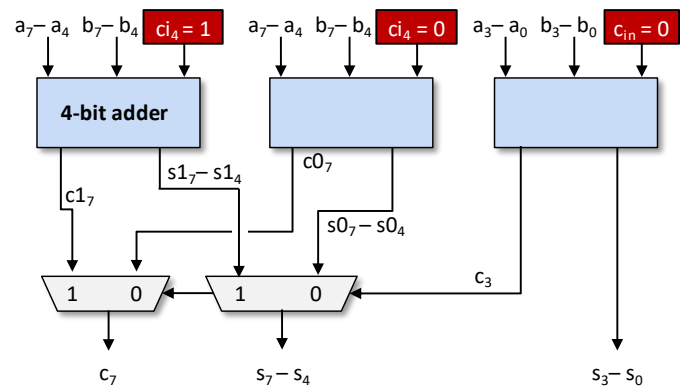
 
## 1.5 QUESTION 5

Model a design using HDL that can count the number of 1s in an 4-bit binary number. For example, the 4'b0101 should output 3'b010. The definition of the module is given below.


```
module count_1 (
    input logic [3:0] a,
    output logic [2:0] out
);
    // ...
    // Add your description here
    // ...
endmodule
```


 
## 1.6 QUESTION 5

Model a design using HDL that can count the number of 0s in an 4-bit binary number. For example, the 4'b0001 should output 3'b011. The definition of the module is given below.


```
module count_0 (
    input logic [3:0] a,
    output logic [2:0] out
);
    // ...
    // Add your description here
    // ...
endmodule
```


 
## 1.7 QUESTION 7

Model a design in HDL that has one 8-bit input, a 3-bit control input, and eight 8-bit outputs. The value from the input should be assigned to the corresponding output based on the 2-bit control value, while the other three outputs are set to zero. The definition of the module is given below.


```
module switchbox (
    input logic [7:0] a,
    input logic [2:0] ctrl,
    output logic [7:0] out1,out2,out3,out4,out5,out6,out7,out8
);
    // ...
    // Add your description here
    // ...
endmodule
```



## 1.8 QUESTION 8

Model using HDL a design that uses a **16-to-1 multiplexer** and implements a 4-bit binary to gray encoder. The gray encoding can be seen in the following table. The module definition is also seen below.

| <i>Decimal</i> | <b>Binary</b> | <b>Gray</b> |
|----------------|---------------|-------------|
| 0              | 0000          | 0000        |
| 1              | 0001          | 0001        |
| 2              | 0010          | 0011        |
| 3              | 0011          | 0010        |
| 4              | 0100          | 0110        |
| 5              | 0101          | 0111        |
| 6              | 0110          | 0101        |
| 7              | 0111          | 0100        |
| 8              | 1000          | 1100        |
| 9              | 1001          | 1101        |
| 10             | 1010          | 1111        |
| 11             | 1011          | 1110        |
| 12             | 1100          | 1010        |
| 13             | 1101          | 1011        |
| 14             | 1110          | 1001        |
| 15             | 1111          | 1000        |

 

```

module bin2gray (
    input  logic [3:0] binary,
    output logic [3:0] bcd
);

    // ...
    // Add your description here
    // ...

endmodule

```